



→ Energy Gap : ① Conductors :  $E_g = 0$   
 ② Semi- ( :  $E_g < 3\text{eV}$   
 ③ Insulators :  $E_g > 3\text{eV}$

$$I_e = I_c + I_b$$

$$\alpha = \frac{I_c}{I_e}$$

$$\beta = \frac{I_c}{I_b}$$

① Forward Biasing : Reverse Biasing

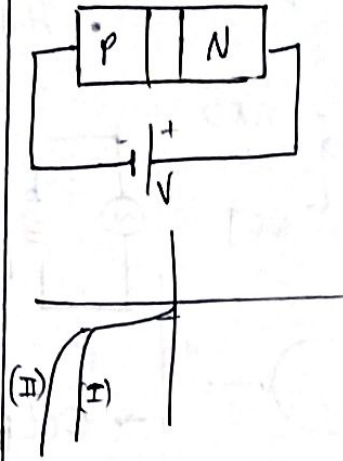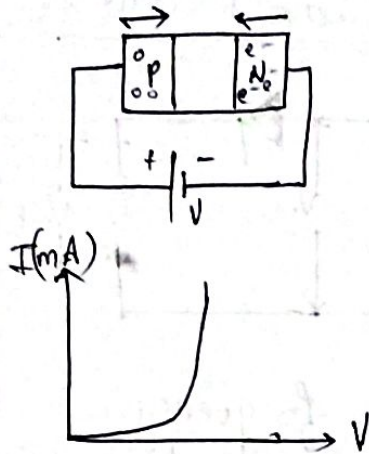

# Diode : Non-ohmic conductors

# Ideal  $r_f \approx 0$

$I \rightarrow$  Zener Break  
 $I \rightarrow$  Avalanche Break

# Ideal  $r_f \Rightarrow \infty$

Rectifiers

$$\eta = \frac{I_{avg}^2 R_L}{I_{rms}^2 (r_f + R_L)}$$

$$\gamma = \sqrt{\frac{(I_{rms})^2}{(I_{avg})^2} - 1}$$

① Half wave .R

$$\eta = \frac{0.406}{\left(1 + \frac{r_f}{R_L}\right)}$$

$$\eta_{max} = 0.406$$

$$\% \eta_{max} = 41.6\%$$

$$\gamma = 1.21$$

$$f = 1.57$$

② Full wave .R

$$\eta = \frac{0.812}{\left(1 + \frac{r_f}{R_L}\right)}$$

$$\eta_{max} = 0.812$$

$$\% \eta_{max} = 81.2\%$$

$$\gamma = 0.48$$

$$f = 1.11$$

$$\alpha_{dc} = \frac{\beta_{dc}}{\beta_{dc} + 1}$$

$$\beta_{dc} = \frac{\alpha_{dc}}{1 - \alpha_{dc}}$$

→ LED

(AlGaAs) → I.R

(GaAsP) → Red or Yellow

(AlGaP) → Red or Green

(ZnSe)  
(SiC) → Blue Light

Al → Aluminium  
 P → Phosphide  
 Se → Selenide  
 Ga → Gallium

Si → Silicon  
 C → Carbide

Zener diode



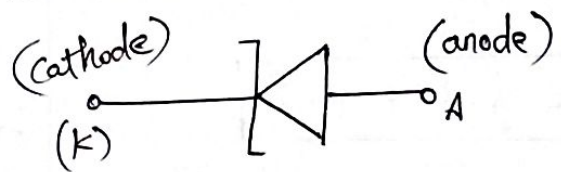


Photo diode :

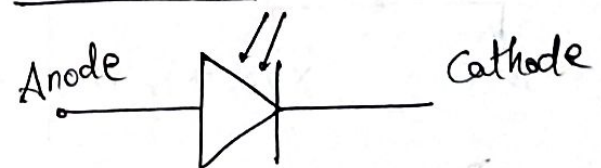

Light Emitting diode [LED] :

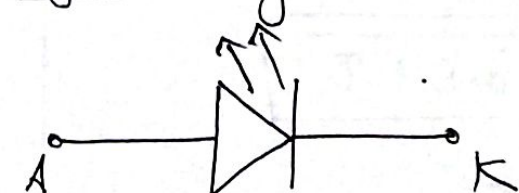




# LOGIC


① OR

$$Y = A + B$$

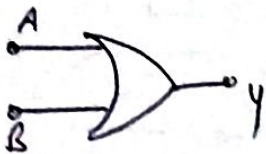

② AND

$$Y = A \cdot B$$

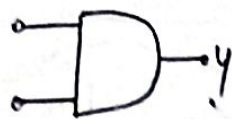


③ NOT

$$Y = \bar{A}$$




$$\text{Ripple factor} = \frac{\text{r.m.s. of AC component}}{\text{Value of DC Component}}$$

• Half wave Rectifier:

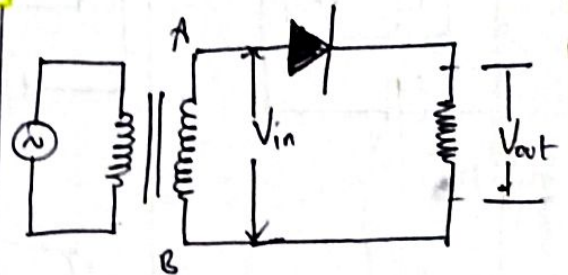

→ Output frequency is same as that of input.

④ NOR

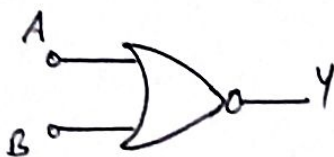


$$Y = \overline{A + B}$$

⑤ NAND



$$Y = \overline{A \cdot B}$$


Full wave Rectifier

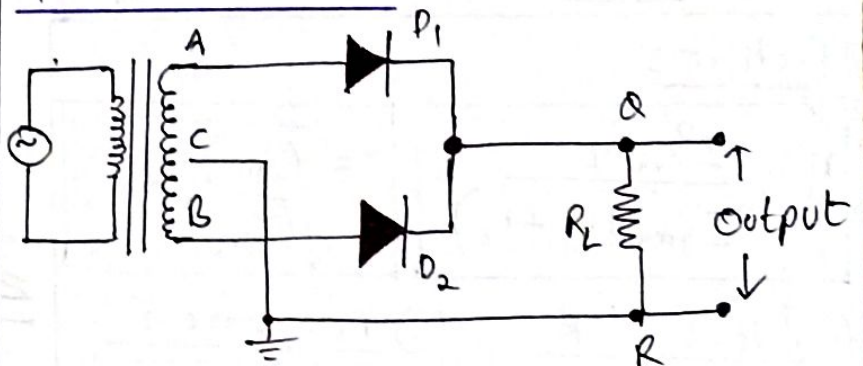

→ Output frequency is twice that of input frequency.



⑥ Ex-OR

2 NOT + 2 AND + one OR

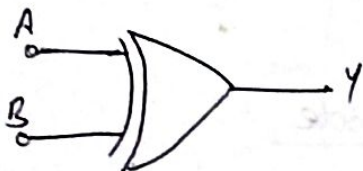

$$Y = \bar{A} \cdot B + \bar{B} \cdot A$$

⑦ Ex-NOR

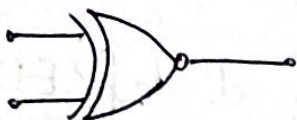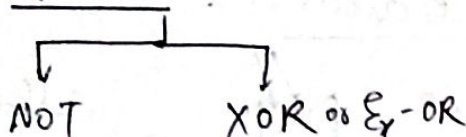

$$Y = \overline{\bar{A} \cdot B + \bar{B} \cdot A}$$